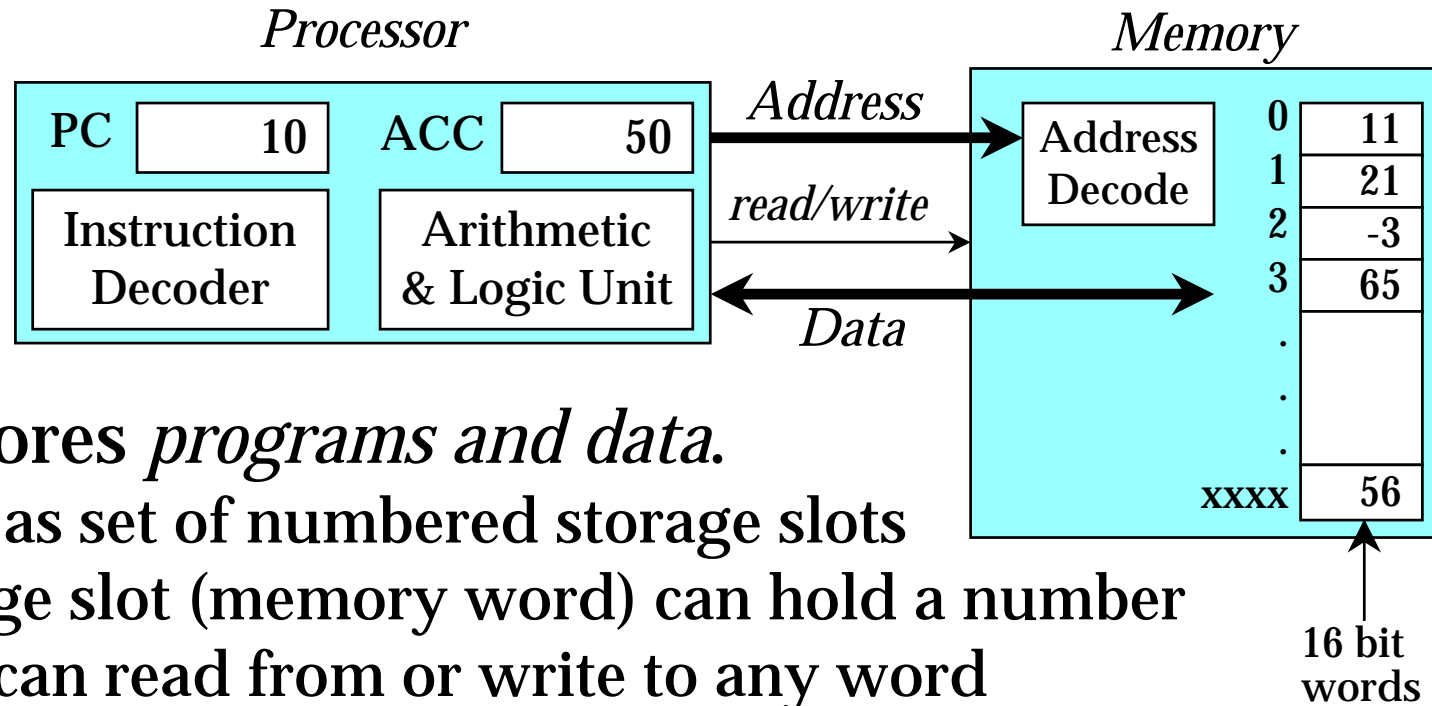


Introduction to Computer Design

- Review of simple processor and memory
- Fetch and execute cycle
- Processor organization
- Executing instructions
- Processor implementation

Basic Processor & Memory



- Memory stores *programs and data*.
 - » organized as set of numbered storage slots
 - » each storage slot (memory word) can hold a number
 - » processor can read from or write to any word
- Fetch & execute cycle
 - » read word whose address is in *Program Counter* (PC) and increment PC
 - » interpret stored value as *instruction* (decoding)
 - » perform instruction using *Accumulator* (ACC) and *Arithmetic & Logic Unit* (ALU)

Simple Instruction Set


0xxx	load <i>ACC</i> with value stored in memory word xxx
1xxx	store value in <i>ACC</i> into memory word xxx
2xxx	add value in memory word xxx to value in <i>ACC</i>
3000	negate the value in <i>ACC</i>
3001	halt
4xxx	change the value of <i>PC</i> to xxx
5xxx	if the value of <i>ACC</i> is zero, change <i>PC</i> value to xxx
6xxx	load <i>ACC</i> with value whose address is stored in word xxx
7xxx	store <i>ACC</i> value into word whose address is in word xxx
8xxx	change <i>ACC</i> value to xxx
9xxx	add xxx to the value in <i>ACC</i>

Simple Program

- Add the values in locations 0-9 and write sum in 10.

<u>Address</u>	<u>Instruction</u>	<u>Comment</u>
0010		Store sum here
0011		Pointer to "next" value here
0012 (start)	8000 (load "00")	initialize sum
0013	1010 (store 10)	
0014	1011 (store 11)	initialize pointer
0015 (loop)	8010 (load "10")	if pointer=10, then quit
0016	3000 (negate)	
0017	2011 (add 11)	
0018	5020 (if 0 goto 20)	
0019	6011 (load *11)	sum = sum + *pointer
001a	2010 (add 10)	
001b	1010 (store 10)	
001c	8001 (load "1")	pointer = pointer + 1
001d	2011 (add 11)	
001e	1011 (store 11)	
001f	4015 (goto 15)	
0020 (end)	3001 (halt)	

Execution of a Computer Program

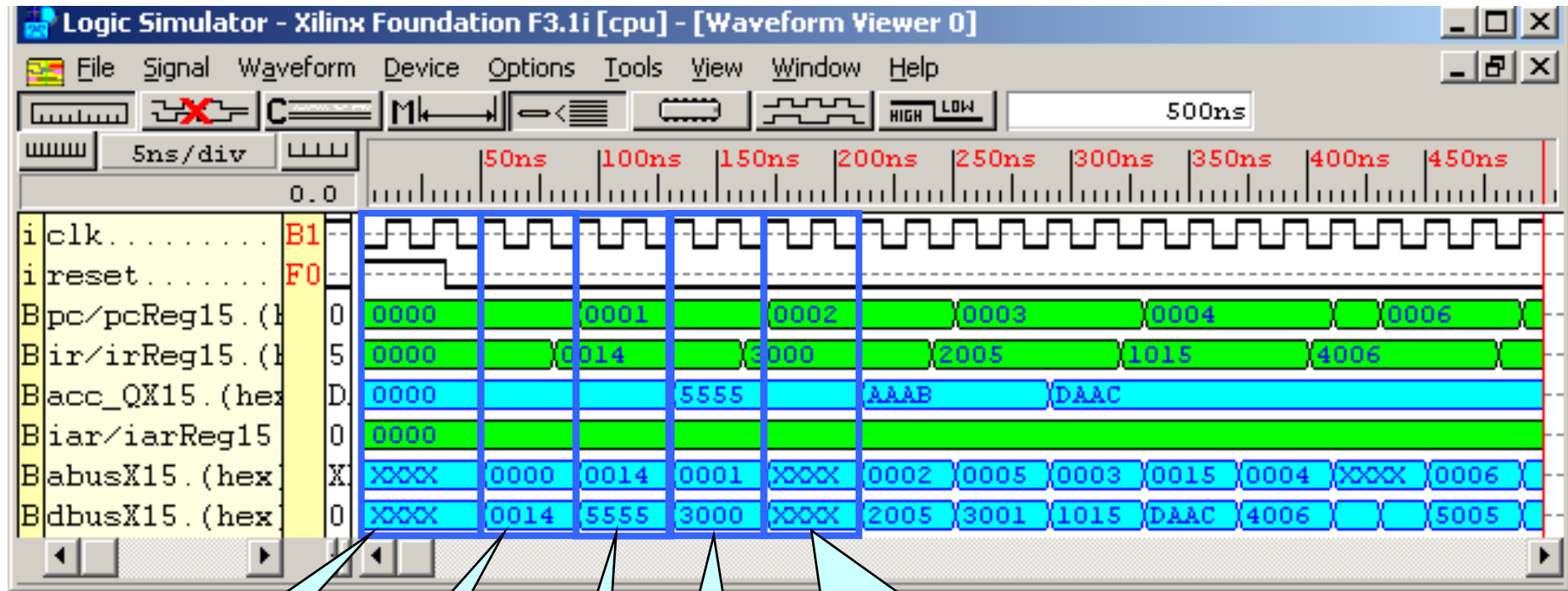

reset
period


fetch first
instruction

execute first
instruction

fetch second
instruction

execute second
instruction

Processing Cycle

 

■ Instruction fetch

- » *PC* used to read word from memory
- » *PC* is incremented

■ Instruction decode

- » first 4 bits of retrieved instruction are decoded to determine what to do
- » appropriate circuitry activated

■ Instruction execution

- » retrieve additional memory words
- » write to memory
- » modify *PC* or *ACC* contents
- » may take different amounts of time to complete

Instruction Execution

■ Load

- » transfer data from memory to *ACC*, using low 12 bits of instruction word as memory address
- » requires asserting of memory signals and *ACC* load signal


■ Conditional branch

- » determine if *ACC*=0
- » if so, transfer low 12 bits of instruction word to *PC*
- » requires assertion of *PC* load signal

■ Indirect store



- » transfer data from memory to Indirect Address Register (*IAR*) using low 12 bits of instruction word as memory address
- » transfer data from *ACC* to memory, using *IAR* contents as address
- » requires assertion of *IAR* load and memory write signals

Processor Block Diagram

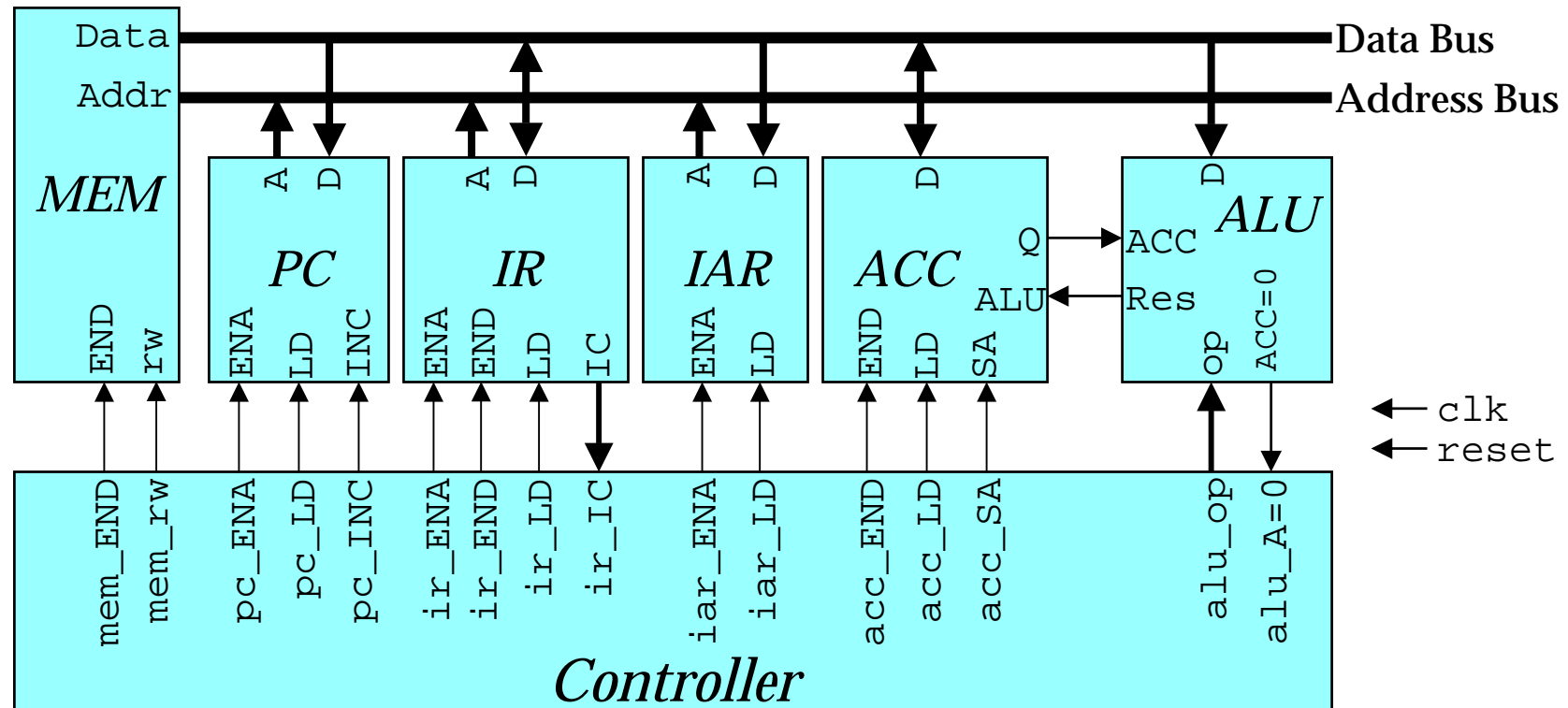


- Processor consists of set of registers, *ALU* & controller.
- Controller contains sequential circuit that asserts control signals needed to fetch & execute instructions.


Tri-State Buffers

  

 - A *tri-state buffer* has a data input and a control input.
 - » when control input is asserted, output equals input
 - » when control input is not asserted, output is disconnected from input - called *high impedance state*
- Tri-state buffers, can be used to build “distributed” multiplexors.
- Shared outputs are called *buses*.
- Also allows single wire to be used as data input and output.




Data Transfer Using Buses

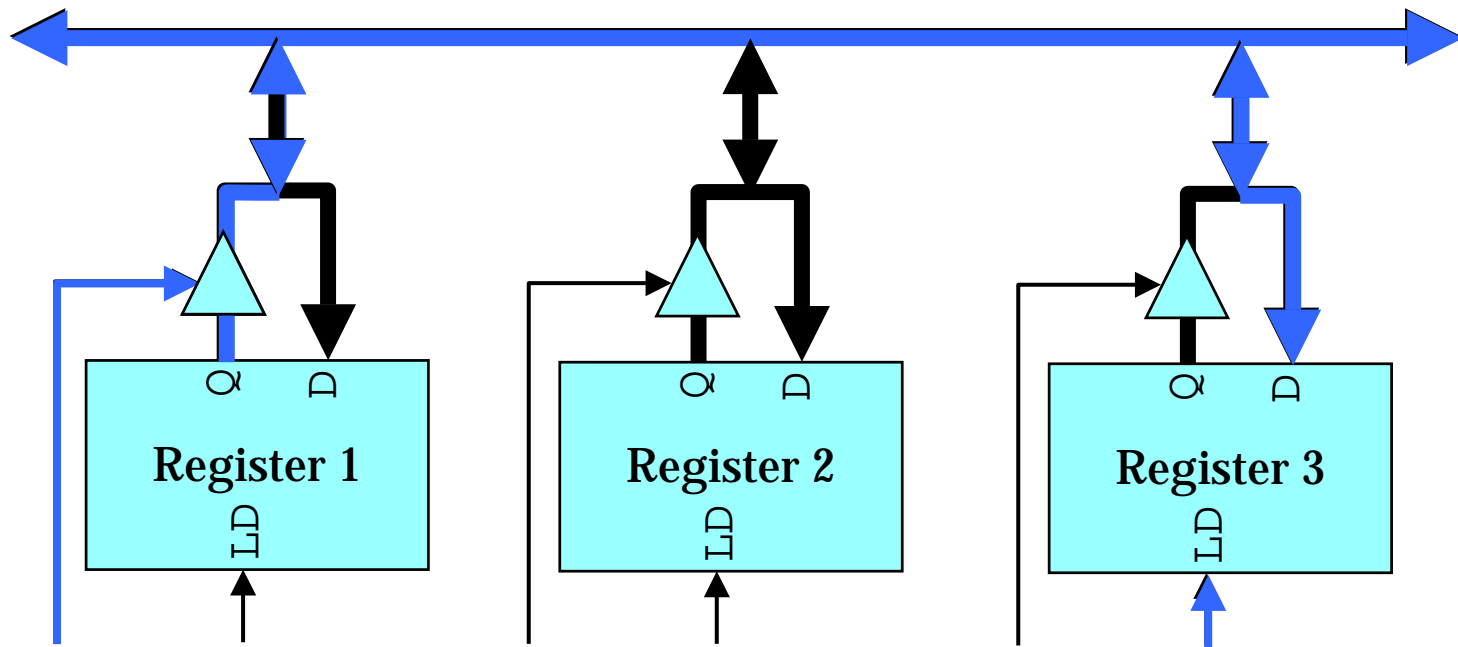


- A *bus* is a shared set of wires used to transfer data among any of several sources/destinations.
- Data transfers involve:
 - » enabling source to place data on the bus
 - » loading data into destination

Program Counter Schematic (4 bit)

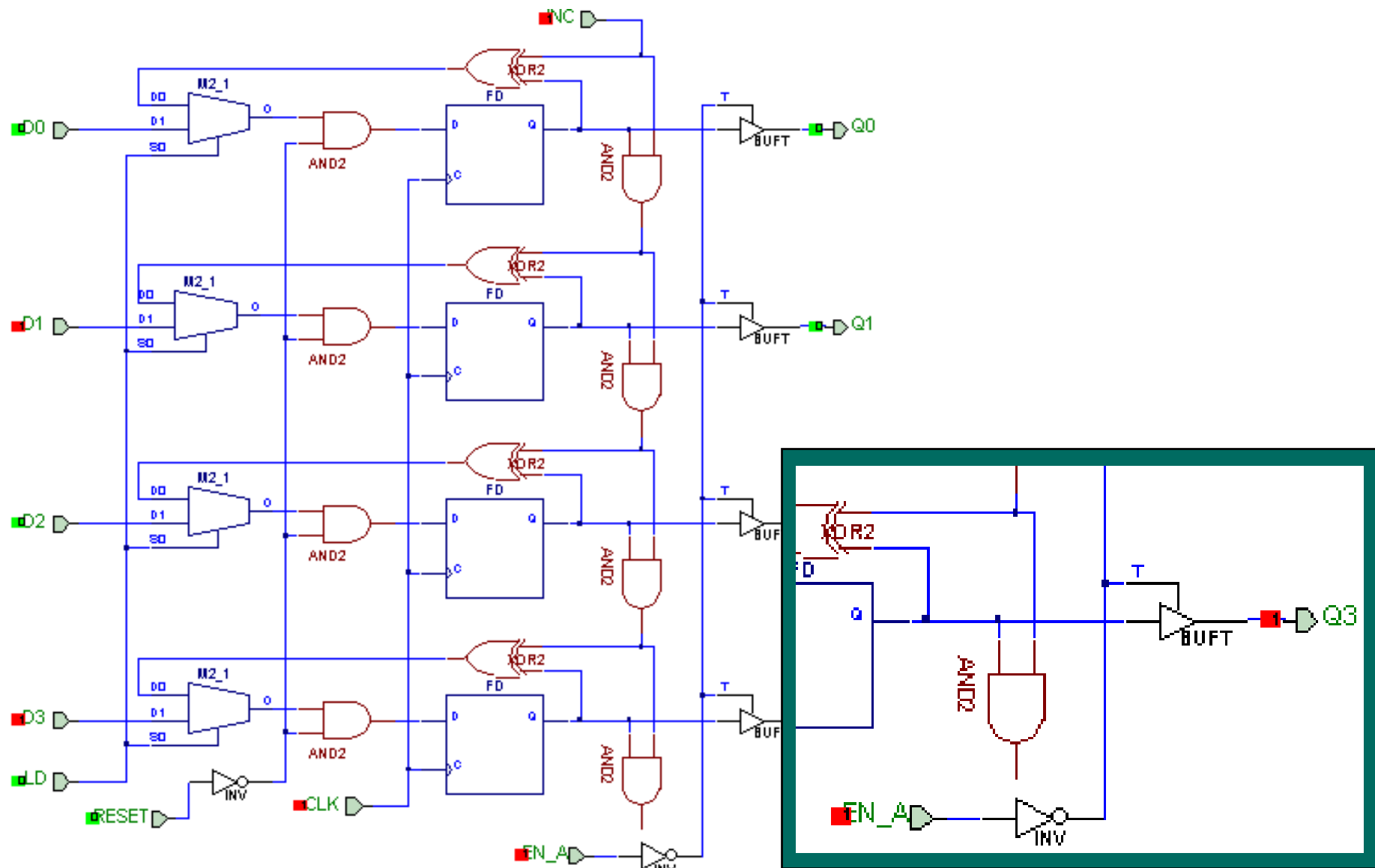


Load Instruction

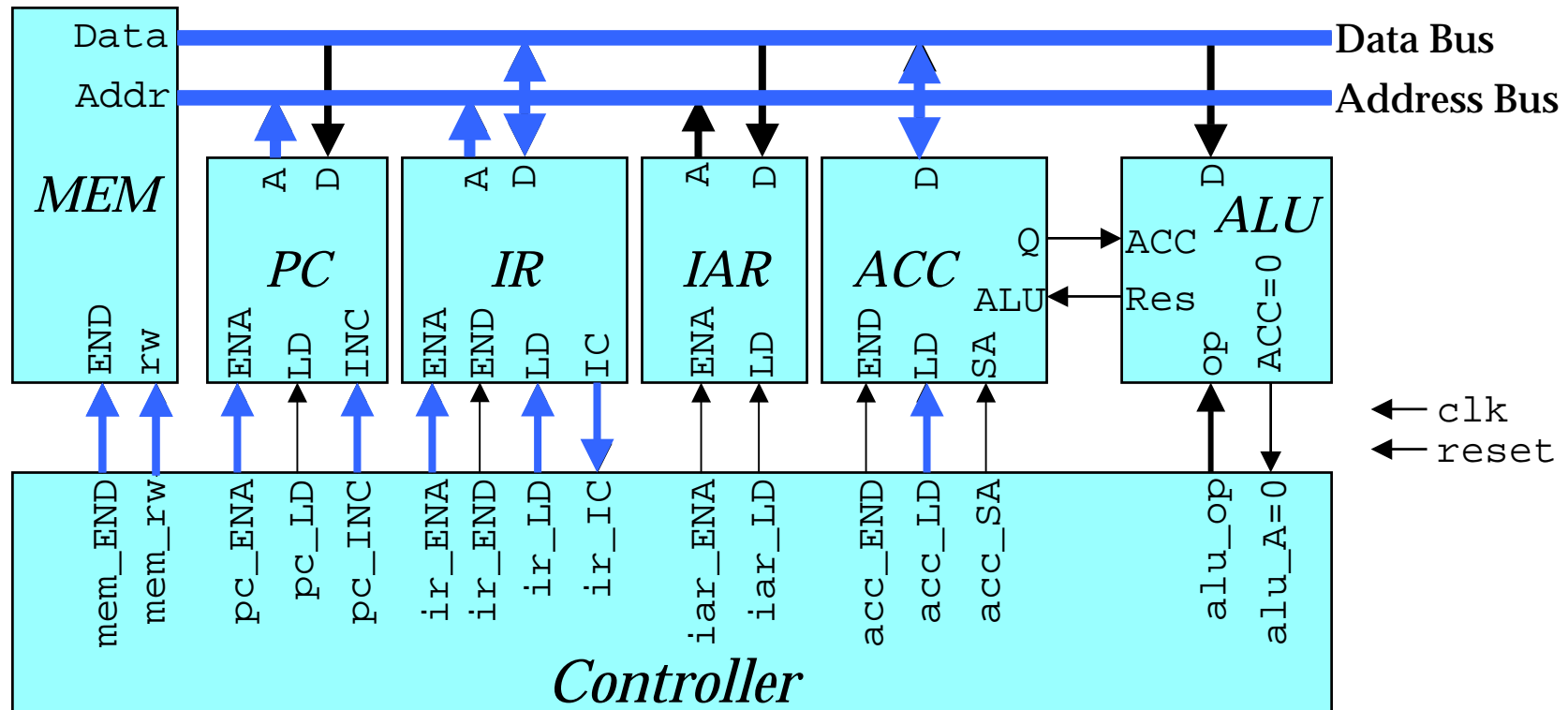

- Fetch instruction and increment PC .
- Transfer data from memory to ACC using low 12 bits of instruction as address

Conditional Branch

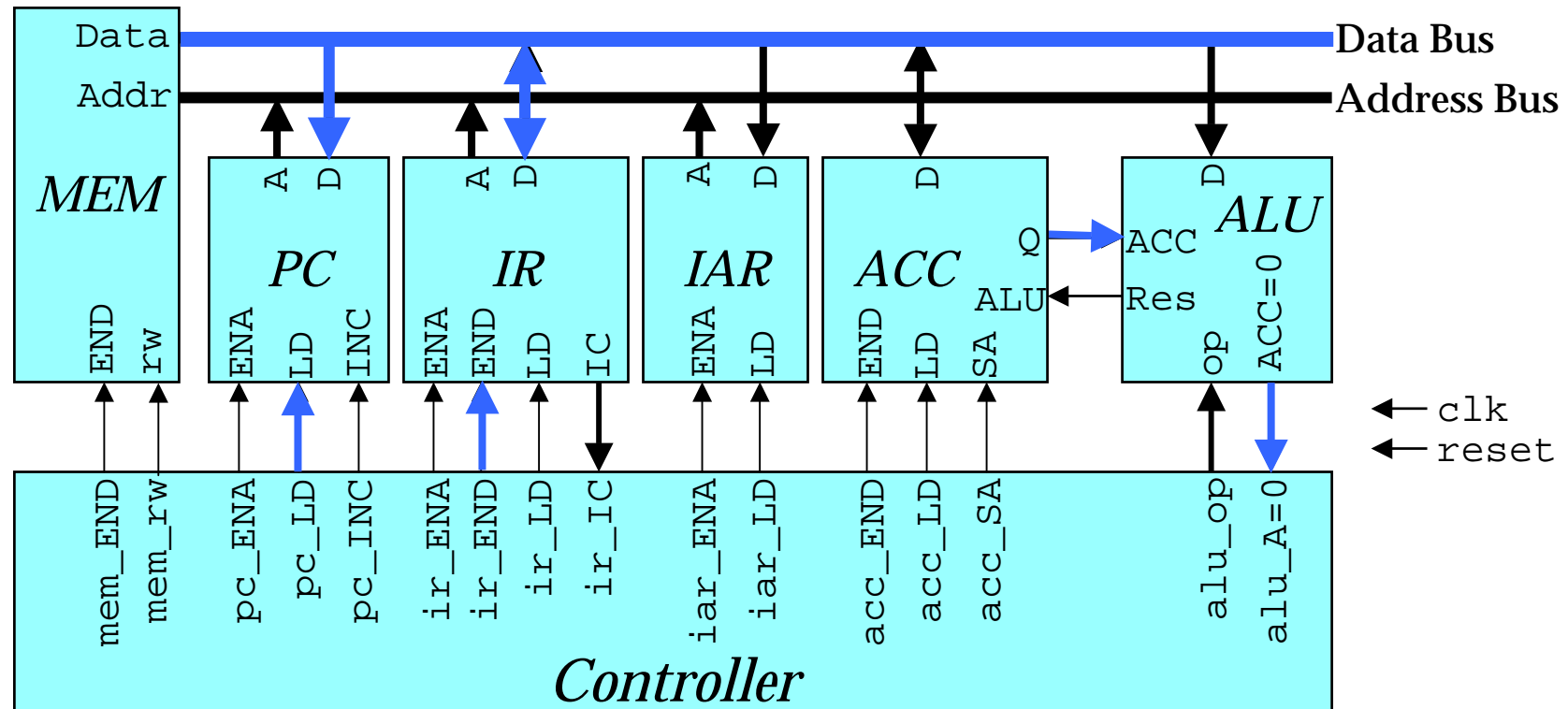


- Determine if $ACC=0$.
- If so, transfer low 12 bits of instruction word to *PC*.

Program Counter

```
entity program_counter is
    port (
        clk, en_A, ld, inc, reset: in STD_LOGIC;
        aBus: out STD_LOGIC_VECTOR(15 downto 0);
        dBus: in STD_LOGIC_VECTOR(15 downto 0)
    );
end program_counter;
architecture pcArch of program_counter is
    signal pcReg: STD_LOGIC_VECTOR(15 downto 0);
begin
    process(clk) begin
        if clk'event and clk = '1' then
            if reset = '1' then
                pcReg <= x"0000";
            elsif ld = '1' then
                pcReg <= dBus;
            elsif inc = '1' then
                pcReg <= pcReg + x"0001";
            end if;
        end if;
    end process;
    aBus <= pcReg when en_A = '1' else "ZZZZZZZZZZZZZZZZZZ";
end pcArch;
```

PC Simulation

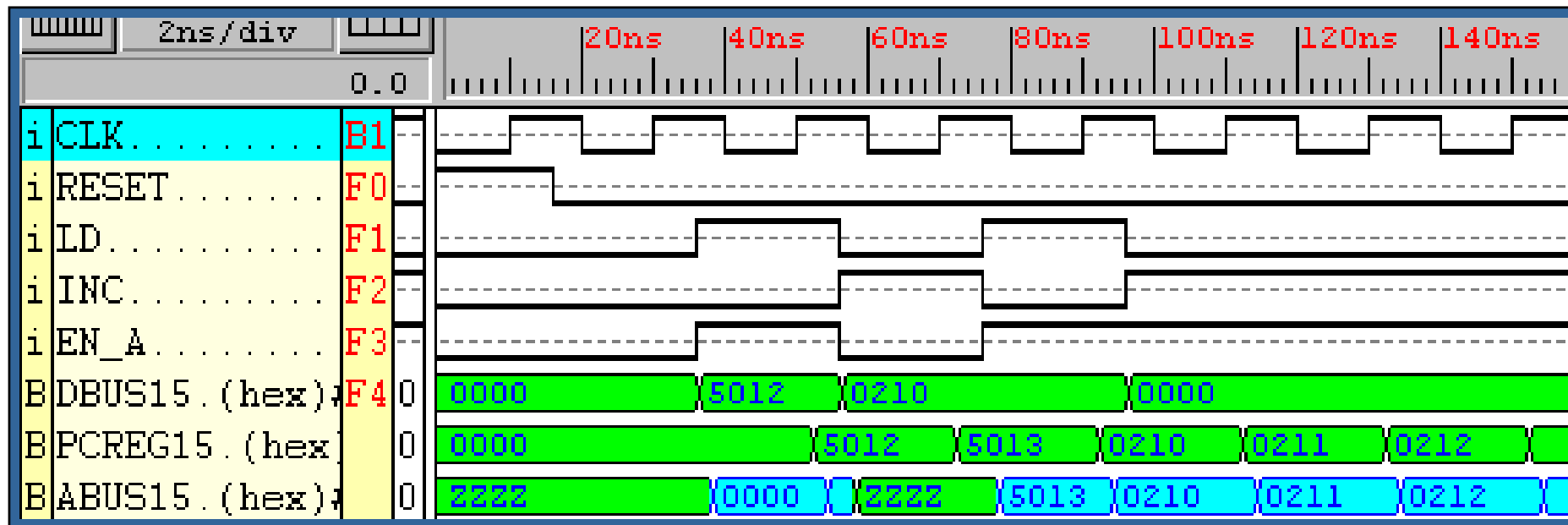

Instruction Register

```
entity instruction_register is
    port (
        clk, en_A, en_D, ld, reset: in STD_LOGIC;
        aBus: out STD_LOGIC_VECTOR(15 downto 0);
        dBus: inout STD_LOGIC_VECTOR(15 downto 0);
        load, store, add, neg, halt, branch: out STD_LOGIC;
        cbranch, iload, istore, mload, madd: out STD_LOGIC
    );
end instruction_register;


architecture irArch of instruction_register is
    signal irReg: STD_LOGIC_VECTOR(15 downto 0);
begin
    process(clk) begin
        if clk'event and clk = '0' then
            if reset = '1' then
                irReg <= x"0000";
            elsif ld = '1' then
                irReg <= dBus;
            end if;
        end if;
    end process;
end process;
```


Instruction Register

```
aBus <= "0000" & irReg(11 downto 0) when en_A = '1' else
    "ZZZZZZZZZZZZZZZZZZ";
dBus <= "0000" & irReg(11 downto 0) when en_D = '1' else
    "ZZZZZZZZZZZZZZZZZZ";

load    <= '1' when irReg(15 downto 12) = x"0"    else '0';
store   <= '1' when irReg(15 downto 12) = x"1"    else '0';
add     <= '1' when irReg(15 downto 12) = x"2"    else '0';
neg     <= '1' when irReg = x"3" & x"000"         else '0';
halt    <= '1' when irReg = x"3" & x"001"         else '0';
branch  <= '1' when irReg(15 downto 12) = x"4"    else '0';
cbranch <= '1' when irReg(15 downto 12) = x"5"    else '0';
iload   <= '1' when irReg(15 downto 12) = x"6"    else '0';
istore  <= '1' when irReg(15 downto 12) = x"7"    else '0';
mload   <= '1' when irReg(15 downto 12) = x"8"    else '0';
madd    <= '1' when irReg(15 downto 12) = x"9"    else '0';
end irArch;
```


I R Simulation

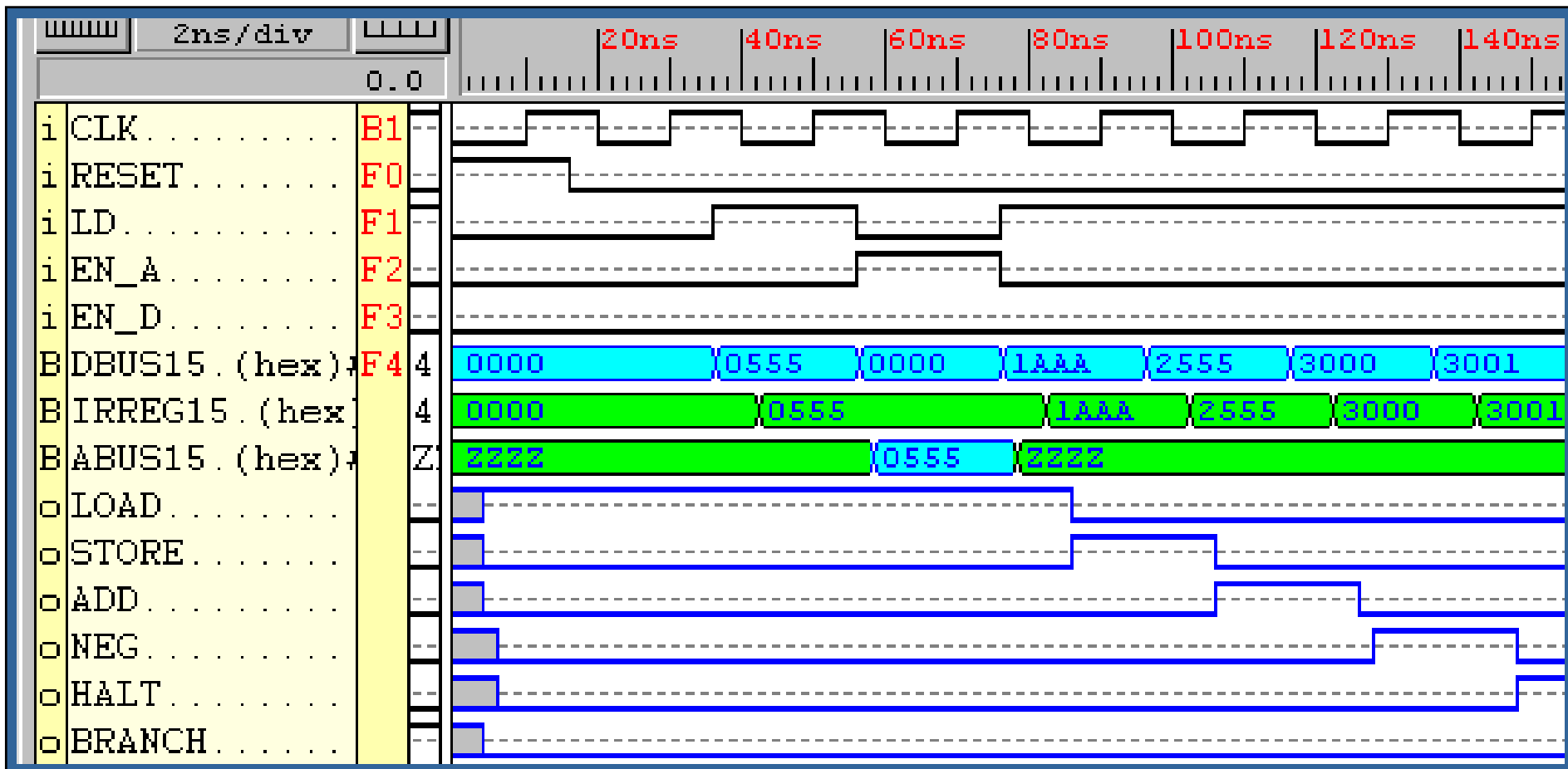

Indirect Address Register

```
entity indirect_addr_register is
    port (
        clk, en_A, ld, reset: in STD_LOGIC;
        aBus: out STD_LOGIC_VECTOR(15 downto 0);
        dBus: in STD_LOGIC_VECTOR(15 downto 0)
    );
end indirect_addr_register;
architecture iarArch of indirect_addr_register is
    signal iarReg: STD_LOGIC_VECTOR(15 downto 0);
begin
    process(clk) begin
        if clk'event and clk = '1' then
            if reset = '1' then
                iarReg <= x"0000";
            elsif ld = '1' then
                iarReg <= dBus;
            end if;
        end if;
    end process;
    aBus <= iarReg when en_A = '1' else
        "ZZZZZZZZZZZZZZZZZZ";
end iarArch;
```


IAR Simulation

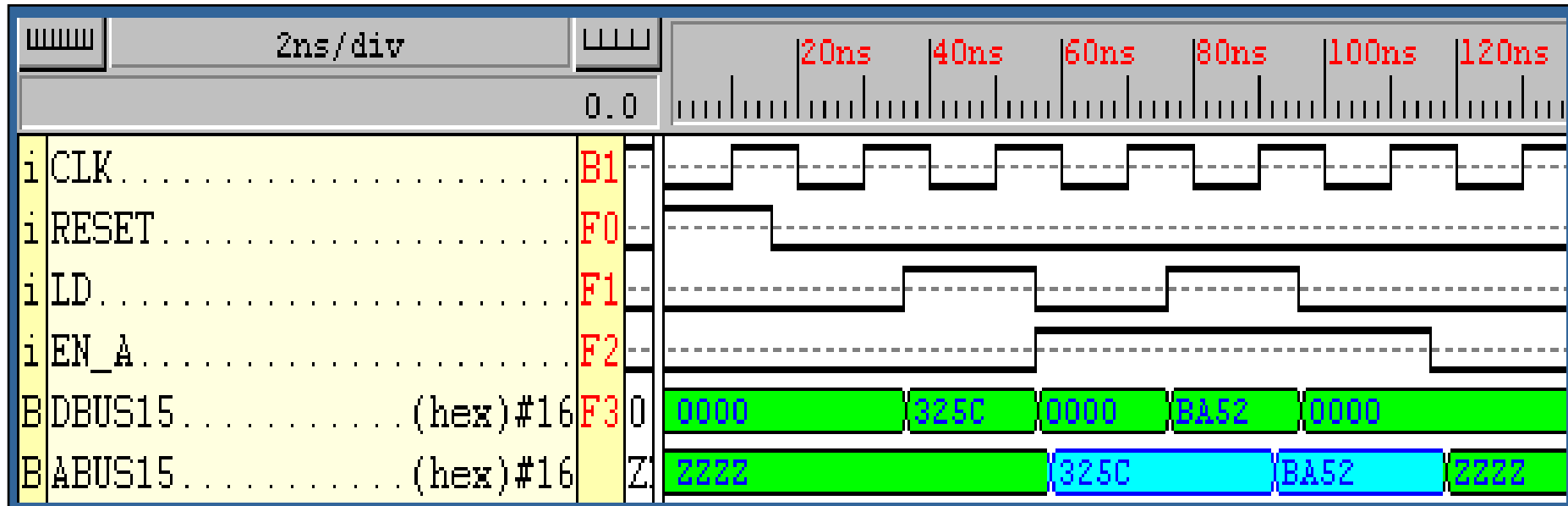

Accumulator

```
entity accumulator is
  port (
    clk, en_D, ld, selAlu, reset: in STD_LOGIC;
    aluD: in STD_LOGIC_VECTOR(15 downto 0);
    dBus, q: inout STD_LOGIC_VECTOR(15 downto 0)
  );
end accumulator;
architecture accArch of accumulator is
  signal accReg: STD_LOGIC_VECTOR(15 downto 0);
begin
  process(clk) begin
    if clk'event and clk = '1' then
      if reset = '1' then
        accReg <= x"0000";
      elsif ld = '1' and selAlu = '1' then
        accReg <= aluD;
      elsif ld = '1' and selAlu = '0' then
        accReg <= dBus;
      end if;
    end if;
  end process;
  dBus <= accReg when en_D = '1' else "ZZZZZZZZZZZZZZZZZZ";
  q <= accReg;
end accArch;
```

ACC Simulation

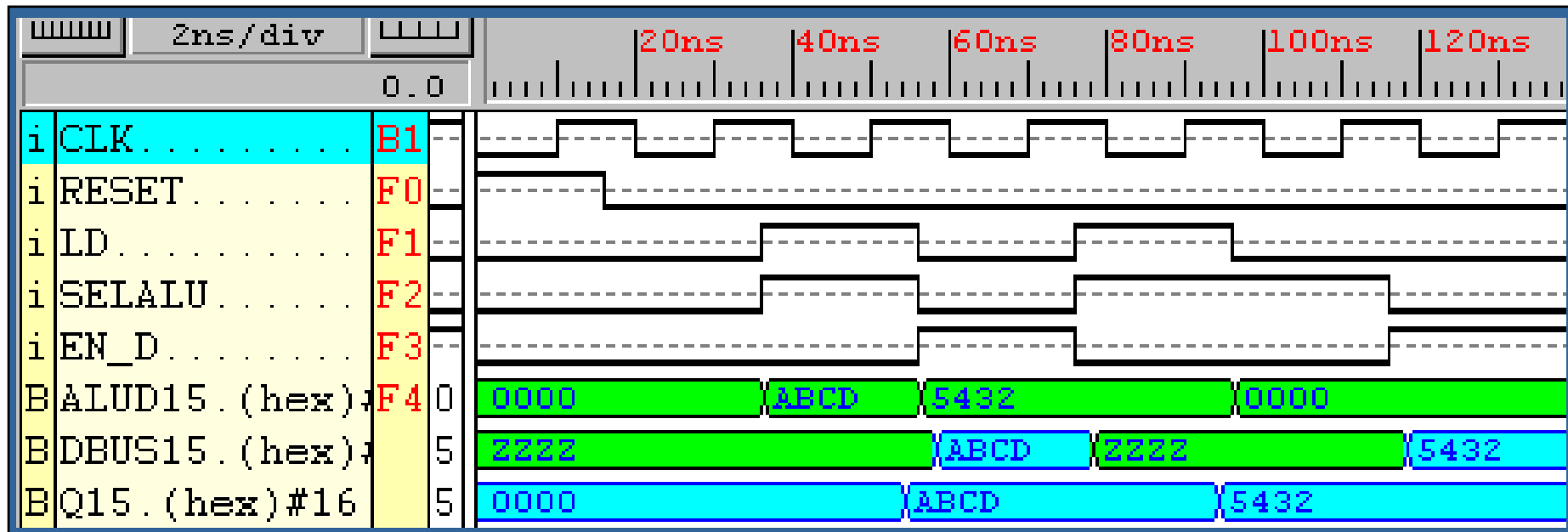


ALU

```
entity alu is
  port (
    op: in STD_LOGIC_VECTOR(1 downto 0);
    accD: in STD_LOGIC_VECTOR(15 downto 0);
    dBus: in STD_LOGIC_VECTOR(15 downto 0);
    result: out STD_LOGIC_VECTOR(15 downto 0);
    accZ: out STD_LOGIC
  );
end alu;

architecture aluArch of alu is
begin
  result <= (not accD) + x"0001" when op = "00" else
    accD + dBus when op = "01" else
    x"0000";
  accZ <= '1' when accD = x"0000" else '0';
end aluArch;
```

ALU Simulation

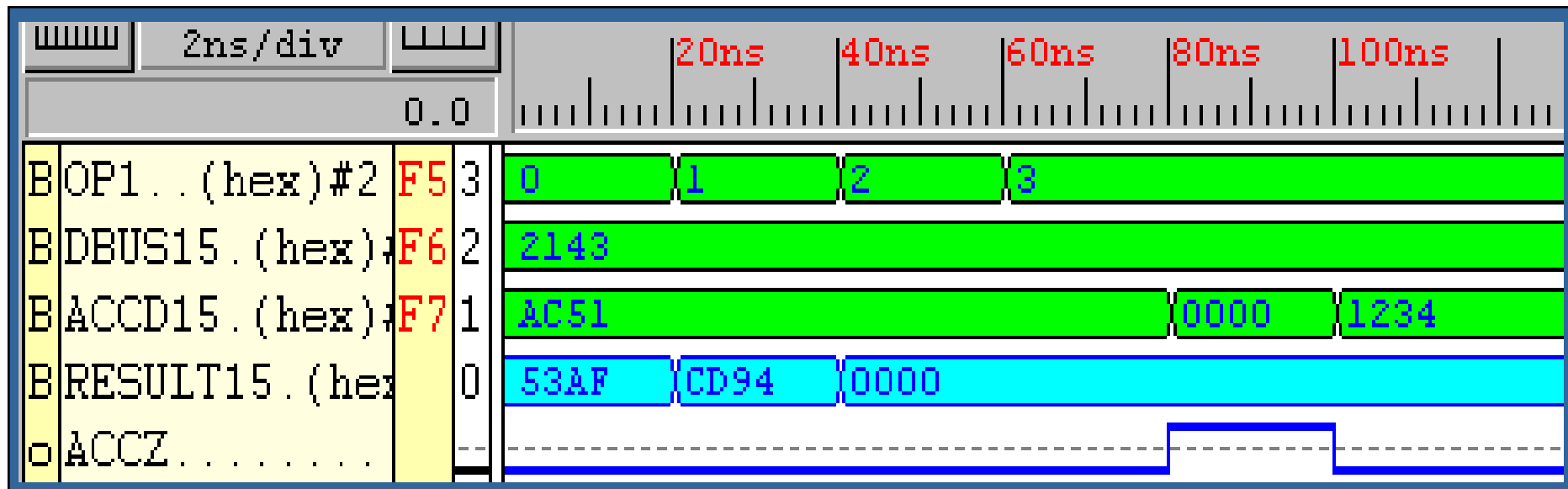

Memory

```
entity ram is
  port (
    r_w, en, reset: in STD_LOGIC;
    aBus: in STD_LOGIC_VECTOR(15 downto 0);
    dBus: inout STD_LOGIC_VECTOR(15 downto 0)
  );
end ram;
architecture ramArch of ram is
  type ram_typ is array(0 to 63) of STD_LOGIC_VECTOR(15 downto 0);
  signal ram: ram_typ;
begin
  process(reset, r_w) begin
    if reset = '1' then
      ram(0)  <= x"4012"; . . . ram(32) <= x"3001";
      for i in 33 to 63 loop
        ram(i) <= x"0000";
      end loop;
    elsif r_w'event and r_w = '0' then
      ram(conv_integer(unsigned(aBus))) <= dBus;
    end if;
  end process;
  dBus <= ram(conv_integer(unsigned(aBus)))when reset = '0'
    and en = '1' and r_w = '1' else "ZZZZZZZZZZZZZZZZZZ";
end ramArch;
```

Memory Simulation

Read Cycle

0.0


20ns

40ns

60ns

80ns

100ns

 

Write Cycle

0.0

20ns


40ns

60ns


80ns

100ns


120ns

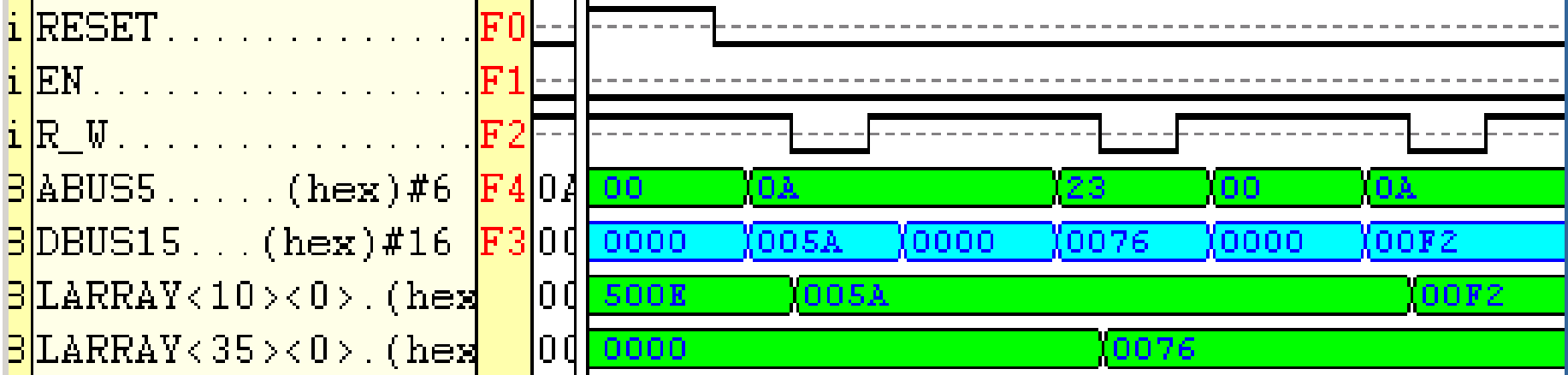

Signal Timing for Controller

 

Signal Timing for Controller

 

Controller

```
entity controller is
  port (
    clk, reset:           in  STD_LOGIC;
    mem_en, mem_rw:       out STD_LOGIC;
    pc_enA, pc_ld, pc_inc: out STD_LOGIC;

    ir_enA, ir_enD, ir_ld: out STD_LOGIC;
    ir_load, ir_store, ir_add: in  STD_LOGIC;
    ir_neg, ir_halt, ir_branch: in  STD_LOGIC;
    ir_cbranch, ir_iloadd: in  STD_LOGIC;
    ir_istore, ir_dload, ir_dadd: in  STD_LOGIC;

    iar_enA, iar_ld:       out STD_LOGIC;
    acc_enD, acc_ld, acc_selAlu: out STD_LOGIC;
    alu_accZ:              in  STD_LOGIC;
    alu_op:                out STD_LOGIC_VECTOR(1 downto 0)
  );
end controller;
```

Controller

```
architecture controllerArch of controller is
type state_type is (reset_state,
    fetch0, fetch1,
    load0, load1,
    store0, store1,
    add0, add1,
    negate0, negate1,
    halt,
    branch0, branch1,
    cbranch0, cbranch1,
    iload0, iload1, iload2, iload3,
    istore0, istore1, istore2, istore3,
    mload0, mload1,
    madd0, madd1
);
signal state: state_type;
```

Controller

```
begin
  process(clk) begin
    if clk'event and clk = '1' then
      if reset = '1' then state <= reset_state;
      else
        case state is
          when reset_state => state <= fetch0;
          when fetch0 => state <= fetch1;
          when fetch1 =>
            if ir_load = '1' then state <= load0;
            elsif ir_store = '1' then state <= store0;
            elsif ir_add = '1' then state <= add0;
            elsif ir_neg = '1' then state <= negate0;
            elsif ir_halt = '1' then state <= halt;
            elsif ir_branch = '1' then state <= branch0;
            elsif ir_cbranch = '1' then state <= cbranch0;
            elsif ir_iloadd = '1' then state <= iloadd0;
            elsif ir_istore = '1' then state <= istore0;
            elsif ir_mload = '1' then state <= mload0;
            elsif ir_madd = '1' then state <= madd0;
            end if;
          when load0 => state <= load1;
          when load1 => state <= fetch0;
          -- yada yada yada
        end if;
      end if;
    end if;
  end process;
```

Controller

```
process begin -- special process for memory write timing
    wait until clk = '0';
    if state = store0 or state = istore2 then
        mem_rw <= '0';
    else
        mem_rw <= '1';
    end if;
end process;

mem_enD <= '1' when
    state =  fetch0 or state =  fetch1 or
    state =   load0 or state =   load1 or
    state =    add0 or state =    add1 or
    state =  iload0 or state =  iload1 or
    state =  iload2 or state =  iload3 or
    state = istore0 or state = istore1
else '0';


pc_enA <= '1' when state =  fetch0 or state =  fetch1
else '0';

pc_ld <= '1'  when state = branch0 or (state = cbranch0 and alu_accZ = '1')
else '0';


pc_inc <= '1' when state =  fetch1
else '0';

-- yada yada yada
end controllerArch;
```



Processor Simulation

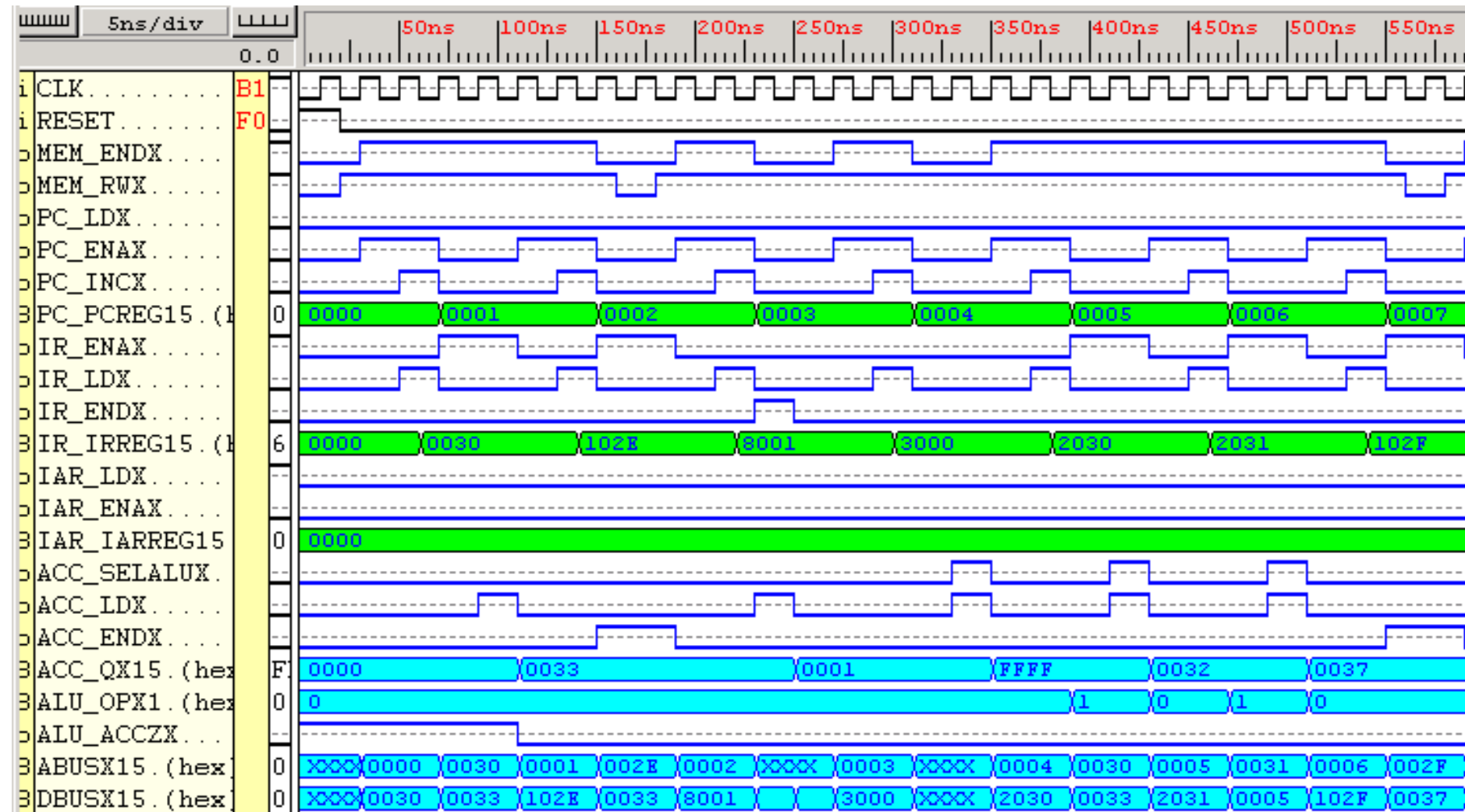

Processor Simulation

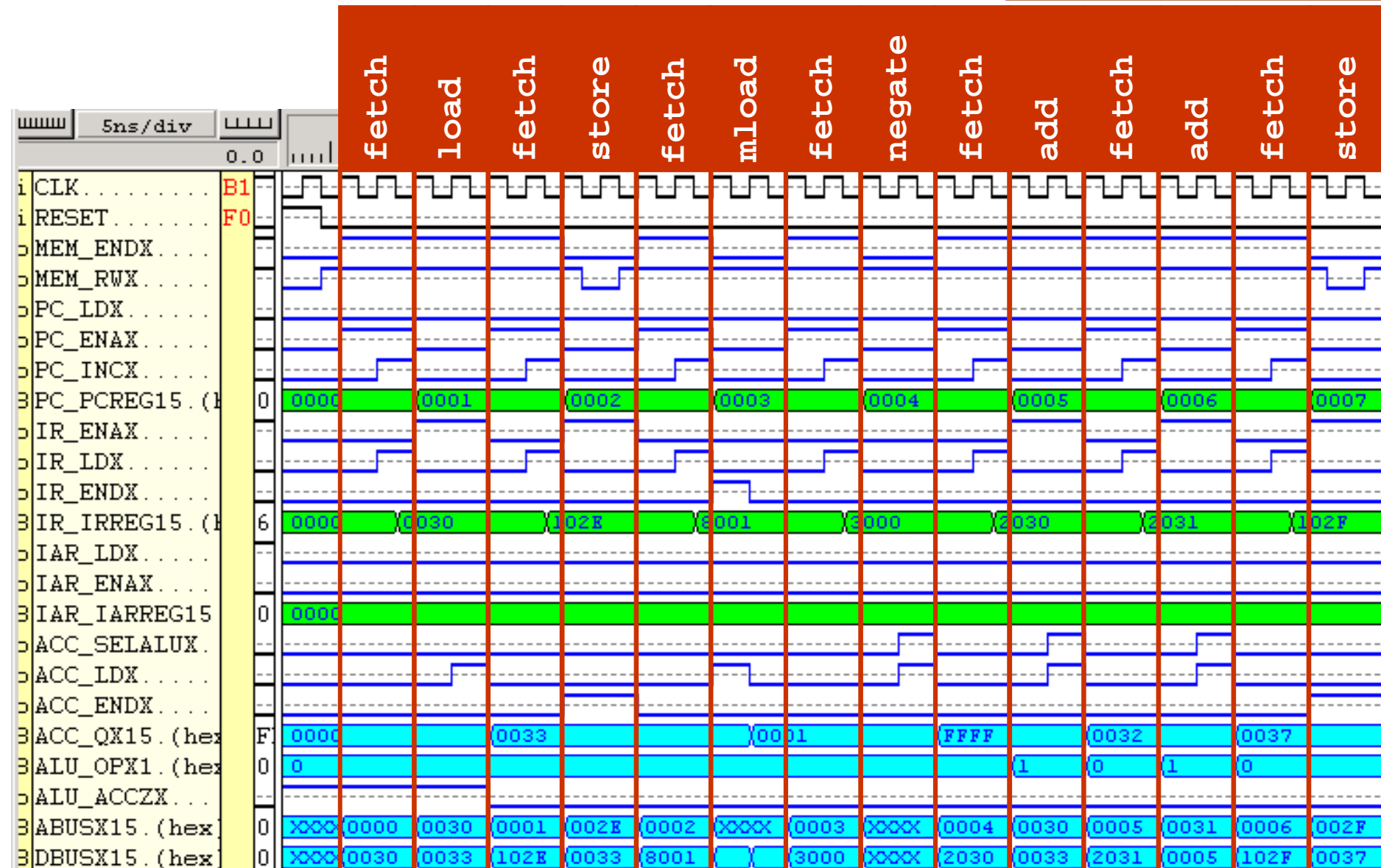 

Processor Simulation



Processor Simulation

